



Vidyavardhini's College of Engineering and Technology

Department of Artificial Intelligence & Data Science

Experiment No. 2
Basic gates using universal gates.
Name:Ayush Mayekar
Roll Number:28
Date of Performance:
Date of Submission:



Vidyavardhini's College of Engineering and Technology

Department of Artificial Intelligence & Data Science

Aim - To realize the gates using universal gates.

Objective -

- 1) To study the realization of basic gates using universal gates.
- 2) Understanding how to construct any combinational logic function using NAND or NOR gates only.

Theory -

AND, OR, NOT are called basic gates as their logical operation cannot be simplified further. NAND and NOR are called universal gates as using only NAND or only NOR, any logic function can be implemented.

Components required -


1. IC's 7400(NAND) 7402(NOR)
2. Bread Board.
3. Connecting wires.

Circuit Diagram -




Vidyavardhini's College of Engineering and Technology

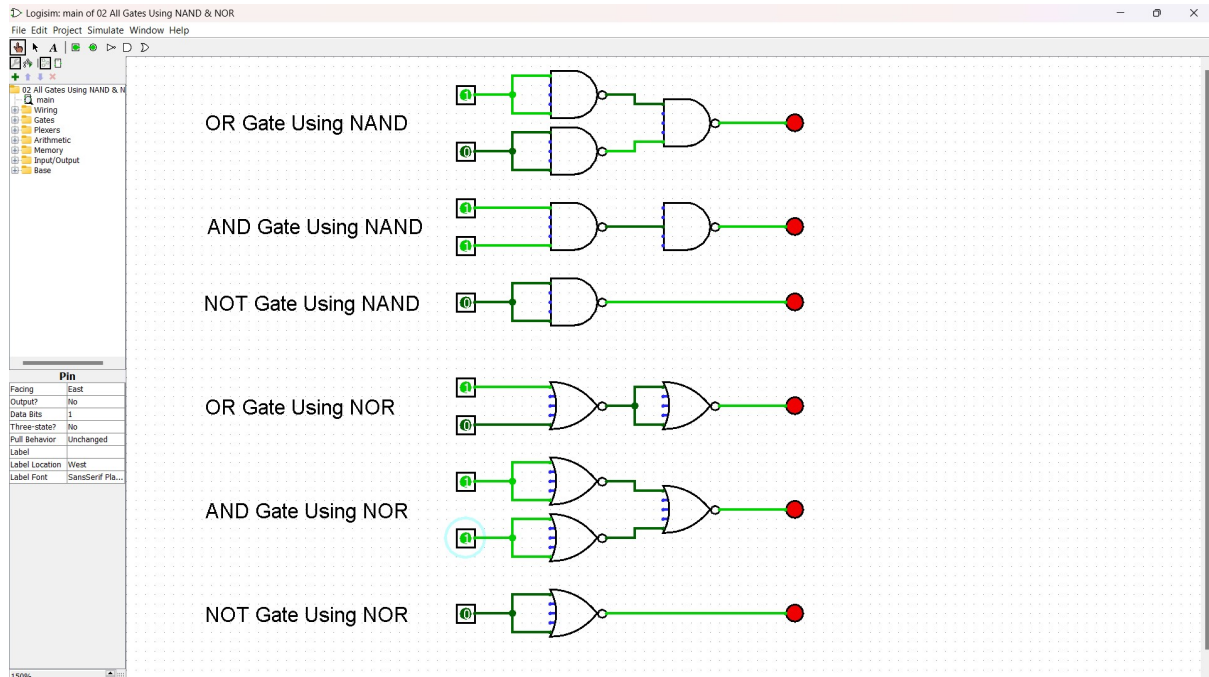Department of Artificial Intelligence & Data Science




Implementation using NAND gate:

(a) NOT gate: $Y = A'$

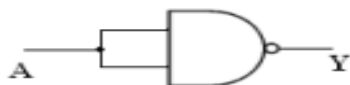


A	Y
0	1
1	0

(b) AND gate: $Y = A \cdot B$

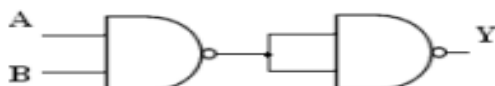


A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

(c) OR gate: $Y = A + B$

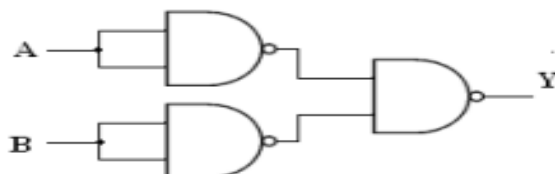

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

(d) NOR gate: $Y = (A + B)'$

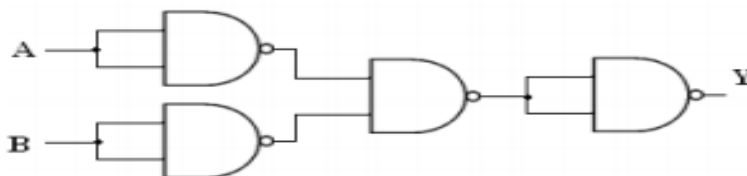


A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0



Vidyavardhini's College of Engineering and Technology

Department of Artificial Intelligence & Data Science


(e) Ex-OR gate: $Y = A \oplus B$

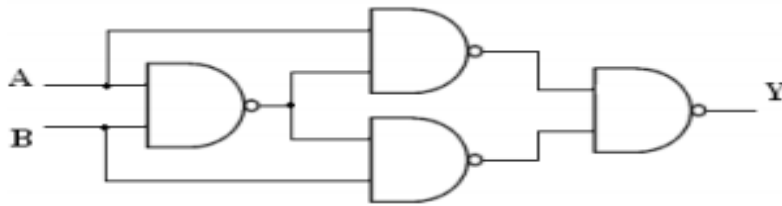

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0


Implementation using NOR gate:

(a) NOT gate: $Y = A'$

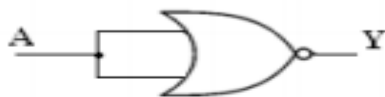


A	Y
0	1
1	0

(b) AND gate: $Y = A \cdot B$

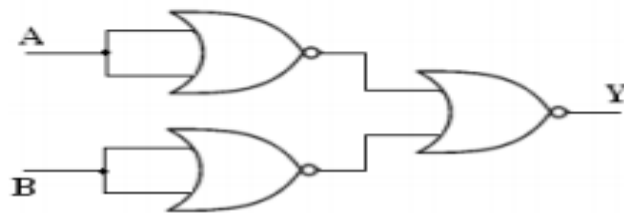


A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

(c) OR gate: $Y = A + B$

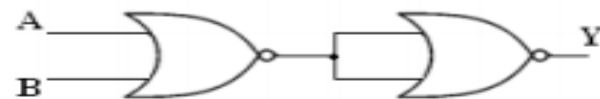


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

(d) NAND gate: $Y = (AB)'$

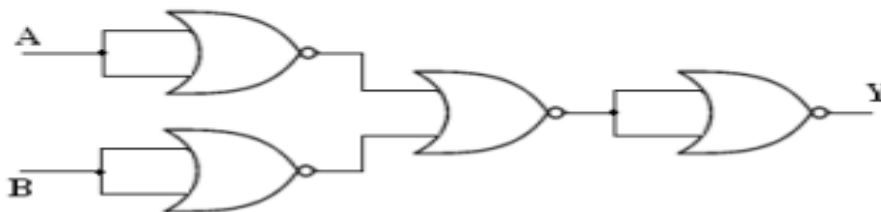

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

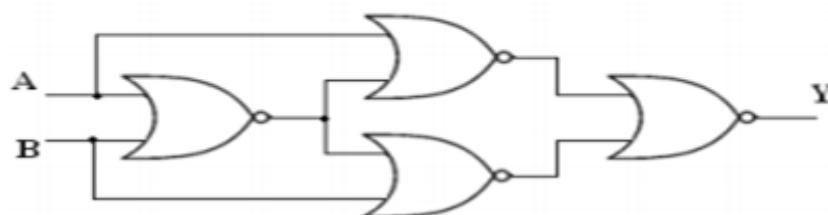(e) Ex-NOR gate: $Y = A \odot B = (A \oplus B)'$



A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1



Vidyavardhini's College of Engineering and Technology

Department of Artificial Intelligence & Data Science

Procedure:

- a) Connections are made as per the circuit diagrams.
- b) By applying the inputs, the outputs are observed and the operations are verified with the help of truth table.

Conclusion -

The experiment carried out on universal gates within the Logisim platform has furnished us with invaluable insights into the adaptability and functionality of these fundamental digital logic components. Through this experiment, we've showcased the remarkable capacity of universal gates to execute a diverse spectrum of logical operations, thus emphasizing their pivotal role in contemporary digital circuit design. This investigation serves as a clear testament to the significance of comprehending and harnessing the potential of universal gates within the realm of digital electronics, offering a path to crafting circuitry that is not only more efficient but also highly versatile.